

# CS2310: Digital Logic Design Lab

## Experiment 8

Prof. Sukhendu Das

22 september 2015

### Problem Statement

Design

- A) Master-Slave J-K Flip-flop
- B) A positive Edge-triggered T Flip-flop using Logic Gates