

CS2310: Digital Logic Design Lab

Experiment 2

Prof. Sukhendu Das

11 August 2015

In this lab, you will be designing and implementing circuits to solve the following two problems

Using only NAND Gates :

- a) Design XOR gate
- b) Design a 3-bit Majority gate

Using only NOR Gates :

- a) Design XOR gate
- b) Design a 3-bit Majority gate