

CS2310: Digital Logic Design Lab

Experiment 5

Prof.Sukhendu Das

1 September 2015

Problem Statement

There are 16 different airplanes that can land in an airport. Upon landing a plane can park in either Hanger A or in Hanger B. Different airports categorize these planes into the following categories:-

- a. Planes that can park in Hanger A
- b. Planes that can park in Hanger B

Design an optimal circuit that can be installed on the plane to inform the pilot which Hanger to park the plane in. This circuit must work for 2 such airports. Use a 7 segment display to display the input Plane No and a 2:1 Mux to select an airport. Only NAND gates must be used in the circuit.

1) Kolkata Airport

Hanger A – 6,7,8,9,14,15,0,1

Hanger B – 2,3,4,5,10,11,12,13

Chennai Airport

Hanger A – 0,1,2,3,9,11,8,10

Hanger B – 4,5,6,7,12,13,14,15

2) Hyderabad Airport

Hanger A – 4,5,10,11,12,13,2,3

Hanger B – 0,1,6,7,8,9,14,15

Delhi Airport

Hanger A – 1,5,7,9,13,15,3,11

Hanger B – 0,2,4,6,8,10,12,14